

Rhilo Sotto
2/19/2025
COMPE 470L

Lab 4 Report

Introduction

In this lab we design a UART Transmitter with a Clock Scaler to transmit our last name at 9600 bit/s. We implement it in Verilog alongside a testbench to test our Verilog module. The module takes in 8 parallel data bits and transmits them as an 8-bit sequence, alongside a start and a stop bit to indicate when transmission begins and ends.

Verilog Code

UART Transmitter Module

```
module UART_Transmitter #(parameter CLKS_PER_BIT = 10) (  
    input CLK,  
    input data_valid,  
    input [7:0] data_in,  
    output reg active,  
    output reg data_out,  
    output [2:0] cur_state, output [2:0] counter // state and counter  
);  
  
localparam Idle = 3'b000, Start = 3'b001, Data = 3'b010, End = 3'b011;  
reg [2:0] state = Idle;  
reg [2:0] data_counter = 0;  
reg [7:0] internal_data;  
  
// view state and counter as output  
assign cur_state = state;  
assign counter = data_counter;  
  
reg [7:0] BAUD_RATE;  
reg [7:0] Clock_Count;  
reg SEND_BIT;  
  
always @(posedge CLK) begin // CLOCK SCALING  
    if (Clock_Count < CLKS_PER_BIT-1) begin
```

```

        Clock_Count <= Clock_Count + 1;
        SEND_BIT <= 1;
    end
    else begin
        Clock_Count <= 0;
        SEND_BIT <= 0;
    end
end

always @(posedge SEND_BIT) begin // next state logic
    case(state)

        Idle: begin
            state <= (data_valid) ? Start : Idle;
        end

        Start: begin
            state <= Data;
            internal_data <= data_in;
            data_counter <= 0;
        end

        Data: begin
            state <= (data_counter == 7) ? End : Data;
            data_counter <= (data_counter + 1) % 8;
        end

        End: begin
            state <= (data_valid) ? Start : Idle;
        end

        default: state <= Idle;

    endcase
end

always @(*) begin // output logic
    case(state)
        Idle: begin
            data_out <= 1'b1; // idle high
            active <= 1'b0;
        end
        Start: begin
            data_out <= 1'b0; // drops low

```

```
        active <= 1'b1;
    end
    Data: begin
        data_out <= internal_data[data_counter];
    end

    End: begin
        active <= 1'b0;
    end
endcase
end
```

```
endmodule
```

Testbench

```
`timescale 1ns / 1ns
```

```
module tb_UART_Transmitter;
```

```
localparam CLOCK_PERIOD_NS = 10, CLKS_PER_BIT = 2;
```

```
reg CLK = 0;
```

```
always #(CLOCK_PERIOD_NS/2) CLK <= ~CLK;
```

```
reg DV = 0;
```

```
reg [7:0] Di = 8'b00000000;
```

```
wire Active, Do;
```

```
wire [2:0] state, counter;
```

```
UART_Transmitter #(.CLKS_PER_BIT(CCLKS_PER_BIT)) Tx(.CLK(CLK), .data_valid(DV),  
.data_in(Di), .active(Active), .data_out(Do),  
.cur_state(state), .counter(counter));
```

```
initial begin
```

```
/*
```

```
S = 8'b01010011
```

```
O = 8'b01001111
```

```
T = 8'b01010100
```

```
T = 8'b01010100
```

```
O = 8'b01001111
```

```
*/
```

```
#5;
```

```
DV = 1;
```

```
Di = 8'b01010011; // S
```

```
#200;
```

```
Di = 8'b01001111; // O
```

```
#200;
```

```
Di = 8'b01010100; // T
```

```
#200;
```

```
Di = 8'b01010100; // T
```

```
#200;
```

```
Di = 8'b01001111; // O
```


```
#200;
```

```
DV = 0;
```

```
#100;
```

```
    $finish;  
end  
  
endmodule
```

Results

 

Conclusion

In this lab, we designed a UART Transmitter with a Clock Scaler to transmit our last name at 9600 bit/s in Verilog and successfully calculated the required clock cycles per second given a 100MHz clock frequency such as that on the Basys3. I successfully showcased my simulation demo of my last name as transmission bytes in uppercase ASCII, which was transmitted in reverse order serially.