

Rhilo Sotto
3/12/2025
COMPE 470L

Lab 5 Report

Introduction

In this lab we designed a UART Receiver to receive our last name at 9600 bit/s via keystrokes through PuTTY, which sends the 8-bit data package to the UART Transmitter we designed in the previous lab. The transmitter sends back the original keypress as a datastream, which shows up in the PuTTY terminal. We implemented it in Verilog alongside a top level module that included both receiver and transmitter to program into our FPGA. The transmitted stream has 8 data bits, alongside a start and a stop bit to indicate when transmission begins and ends.

Verilog Code

UART Transmitter Module

```
module uart_tx
  #(parameter CLKS_PER_BIT = 10)
  (
    input    i_Clock,
    input    i_Tx_DV,
    input [7:0] i_Tx_Byte,
    output    o_Tx_Active,
    output reg o_Tx_Serial,
    output    o_Tx_Done
  );

  localparam s_IDLE      = 3'b000;
  localparam s_TX_START_BIT = 3'b001;
  localparam s_TX_DATA_BITS = 3'b010;
  localparam s_TX_STOP_BIT  = 3'b011;
  localparam s_CLEANUP     = 3'b100;

  reg [2:0] r_SM_Main = 0;
  reg [14:0] r_Clock_Count = 0;
  reg [2:0] r_Bit_Index = 0;
  reg [7:0] r_Tx_Data = 0;
  reg      r_Tx_Done = 0;
  reg      r_Tx_Active = 0;
```

```

always @(posedge i_Clock)
begin

case (r_SM_Main)
s_IDLE :
begin
o_Tx_Serial  <= 1'b1;      // Drive Line High for Idle
r_Tx_Done    <= 1'b0;
r_Clock_Count <= 0;
r_Bit_Index  <= 0;

if (i_Tx_DV == 1'b1)
begin
r_Tx_Active <= 1'b1;
r_Tx_Data  <= i_Tx_Byte;
r_SM_Main  <= s_TX_START_BIT;
end
else
r_SM_Main <= s_IDLE;
end // case: s_IDLE


// Send out Start Bit. Start bit = 0
s_TX_START_BIT :
begin
o_Tx_Serial <= 1'b0;

// Wait CLKS_PER_BIT-1 clock cycles for start bit to finish
if (r_Clock_Count < CLKS_PER_BIT-1)
begin
r_Clock_Count <= r_Clock_Count + 1;
r_SM_Main    <= s_TX_START_BIT;
end
else
begin
r_Clock_Count <= 0;
r_SM_Main    <= s_TX_DATA_BITS;
end
end // case: s_TX_START_BIT


// Wait CLKS_PER_BIT-1 clock cycles for data bits to finish
s_TX_DATA_BITS :

```

```

begin
  o_Tx_Serial <= r_Tx_Data[r_Bit_Index];

  if (r_Clock_Count < CLKS_PER_BIT-1)
    begin
      r_Clock_Count <= r_Clock_Count + 1;
      r_SM_Main    <= s_TX_DATA_BITS;
    end
  else
    begin
      r_Clock_Count <= 0;

      // Check if we have sent out all bits
      if (r_Bit_Index < 7)
        begin
          r_Bit_Index <= r_Bit_Index + 1;
          r_SM_Main    <= s_TX_DATA_BITS;
        end
      else
        begin
          r_Bit_Index <= 0;
          r_SM_Main    <= s_TX_STOP_BIT;
        end
      end
    end
  end // case: s_TX_DATA_BITS

// Send out Stop bit. Stop bit = 1
s_TX_STOP_BIT :
begin
  o_Tx_Serial <= 1'b1;

  // Wait CLKS_PER_BIT-1 clock cycles for Stop bit to finish
  if (r_Clock_Count < CLKS_PER_BIT-1)
    begin
      r_Clock_Count <= r_Clock_Count + 1;
      r_SM_Main    <= s_TX_STOP_BIT;
    end
  else
    begin
      r_Tx_Done    <= 1'b1;
      r_Clock_Count <= 0;
      r_SM_Main    <= s_CLEANUP;
      r_Tx_Active  <= 1'b0;
    end
  end

```

```

        end
    end // case: s_Tx_STOP_BIT

    // Stay here 1 clock
    s_CLEANUP :
    begin
        r_Tx_Done <= 1'b1;
        r_SM_Main <= s_IDLE;
    end

    default :
        r_SM_Main <= s_IDLE;

    endcase
end

assign o_Tx_Active = r_Tx_Active;
assign o_Tx_Done   = r_Tx_Done;

endmodule

```

UART Receiver Module

```
module uart_rx
  #(parameter CLKS_PER_BIT = 10)
  (
    input    i_Clock,
    input    i_Rx_Serial,
    output   o_Rx_DV,
    output reg [7:0] o_Rx_Byte
  );

  localparam s_IDLE      = 3'b000;
  localparam s_RX_START_BIT = 3'b001;
  localparam s_RX_DATA_BITS = 3'b010;
  localparam s_RX_STOP_BIT  = 3'b011;
  localparam s_CLEANUP      = 3'b100;

  reg      r_Rx_Data_R = 1'b1;
  reg      r_Rx_Data   = 1'b1;

  reg [14:0] r_Clock_Count = 0;
  reg [2:0]  r_Bit_Index   = 0; //8 bits total
  reg [7:0]  r_Rx_Byte     = 0;
  reg      r_Rx_DV        = 0;
  reg [2:0]  r_SM_Main     = 0;

  // Double-register the incoming data.

  // always @(posedge i_Clock)
  // begin
  //   r_Rx_Data_R <= i_Rx_Serial;
  //   r_Rx_Data   <= r_Rx_Data_R;
  // end

  // Control RX state machine
  always @(posedge i_Clock)
    begin

      case (r_SM_Main)
        s_IDLE :
          begin
            r_Rx_DV      <= 1'b0;
            r_Clock_Count <= 0;
          end
      end case
    end
endmodule
```

```

r_Bit_Index  <= 0;

if (i_Rx_Serial == 1'b0)      // Start bit detected
    r_SM_Main <= s_RX_START_BIT;
else
    r_SM_Main <= s_IDLE;
end

// Check middle of start bit to make sure it's still low
s_RX_START_BIT :
begin
    if (r_Clock_Count == (CLKS_PER_BIT-1)/2)
        begin
            if (i_Rx_Serial == 1'b0)
                begin
                    r_Clock_Count <= 0; // reset counter, found the middle
                    r_SM_Main  <= s_RX_DATA_BITS;
                end
            else
                r_SM_Main <= s_IDLE;
            end
        else
            begin
                r_Clock_Count <= r_Clock_Count + 1;
                r_SM_Main  <= s_RX_START_BIT;
            end
        end // case: s_RX_START_BIT

```

```

// Wait CLKS_PER_BIT-1 clock cycles to sample serial data
s_RX_DATA_BITS :
begin
    if (r_Clock_Count < CLKS_PER_BIT-1)
        begin
            r_Clock_Count <= r_Clock_Count + 1;
            r_SM_Main  <= s_RX_DATA_BITS;
        end
    else
        begin
            r_Clock_Count  <= 0;
            o_Rx_Byte[r_Bit_Index] <= i_Rx_Serial;

            // Check if we have received all bits
            if (r_Bit_Index < 7)

```

```

        begin
            r_Bit_Index <= r_Bit_Index + 1;
            r_SM_Main <= s_RX_DATA_BITS;
        end
    else
        begin
            r_Bit_Index <= 0;
            r_SM_Main <= s_RX_STOP_BIT;
        end
    end
end // case: s_RX_DATA_BITS

// Receive Stop bit. Stop bit = 1
s_RX_STOP_BIT :
begin
    // Wait CLKS_PER_BIT-1 clock cycles for Stop bit to finish
    if (r_Clock_Count < CLKS_PER_BIT-1)
        begin
            r_Clock_Count <= r_Clock_Count + 1;
            r_SM_Main <= s_RX_STOP_BIT;
        end
    else
        begin
            r_Rx_DV <= 1'b1;
            r_Clock_Count <= 0;
            r_SM_Main <= s_CLEANUP;
        end
    end
end // case: s_RX_STOP_BIT

// Stay here 1 clock
s_CLEANUP :
begin
    r_SM_Main <= s_IDLE;
    r_Rx_DV <= 1'b0;
end

default :
    r_SM_Main <= s_IDLE;

endcase
end

```

```
assign o_Rx_DV  = r_Rx_DV;  
//assign o_Rx_Byte = r_Rx_Byte;  
  
endmodule // uart_rx
```


UART Top Level Module

```
module uart_tb (
    input clk_100MHz,    // basys 3 FPGA clock signal
    input rx,            // USB-RS232 Rx
    output tx            // USB-RS232 Tx
);

    // 100MHz Clock / 9600 Baudrate = 10417
    localparam c_CLKS_PER_BIT = 10417;

    wire w_Tx_Done, tx_ACTIVE;
    wire rx_DV;
    wire [7:0] w_Rx_Byte;

    uart_rx #(.CLKS_PER_BIT(c_CLKS_PER_BIT)) UART_RX_INST
        (.i_Clock(clk_100MHz),
         .i_Rx_Serial(rx),
         .o_Rx_DV(rx_DV),
         .o_Rx_Byte(w_Rx_Byte)
        );

    uart_tx #(.CLKS_PER_BIT(c_CLKS_PER_BIT)) UART_TX_INST
        (.i_Clock(clk_100MHz),
         .i_Tx_DV(rx_DV),
         .i_Tx_Byte(w_Rx_Byte),
         .o_Tx_Active(tx_ACTIVE),
         .o_Tx_Serial(tx),
         .o_Tx_Done(w_Tx_Done)
        );

endmodule
```

Constraint File

Clock signal

```
set_property PACKAGE_PIN W5 [get_ports clk_100MHz]
```

```
    set_property IOSTANDARD LVCMOS33 [get_ports clk_100MHz]
```

```
    create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports  
clk_100MHz]
```

##USB-RS232 Interface


```
set_property PACKAGE_PIN B18 [get_ports rx]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports rx]
```

```
set_property PACKAGE_PIN A18 [get_ports tx]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports tx]
```

Results

 

Conclusion

In this lab, we learned how to design a UART Receiver to receive our last name at 9600 bit/s in Verilog and successfully calculated the required clock cycles per second for a baud rate of 9600 bit/s, given a 100MHz clock frequency such as that on the Basys3. I successfully showcased my last name in uppercase ASCII in the PuTTY terminal, and learned how to use PuTTY to interface with the Basys3 RX and TX pins.